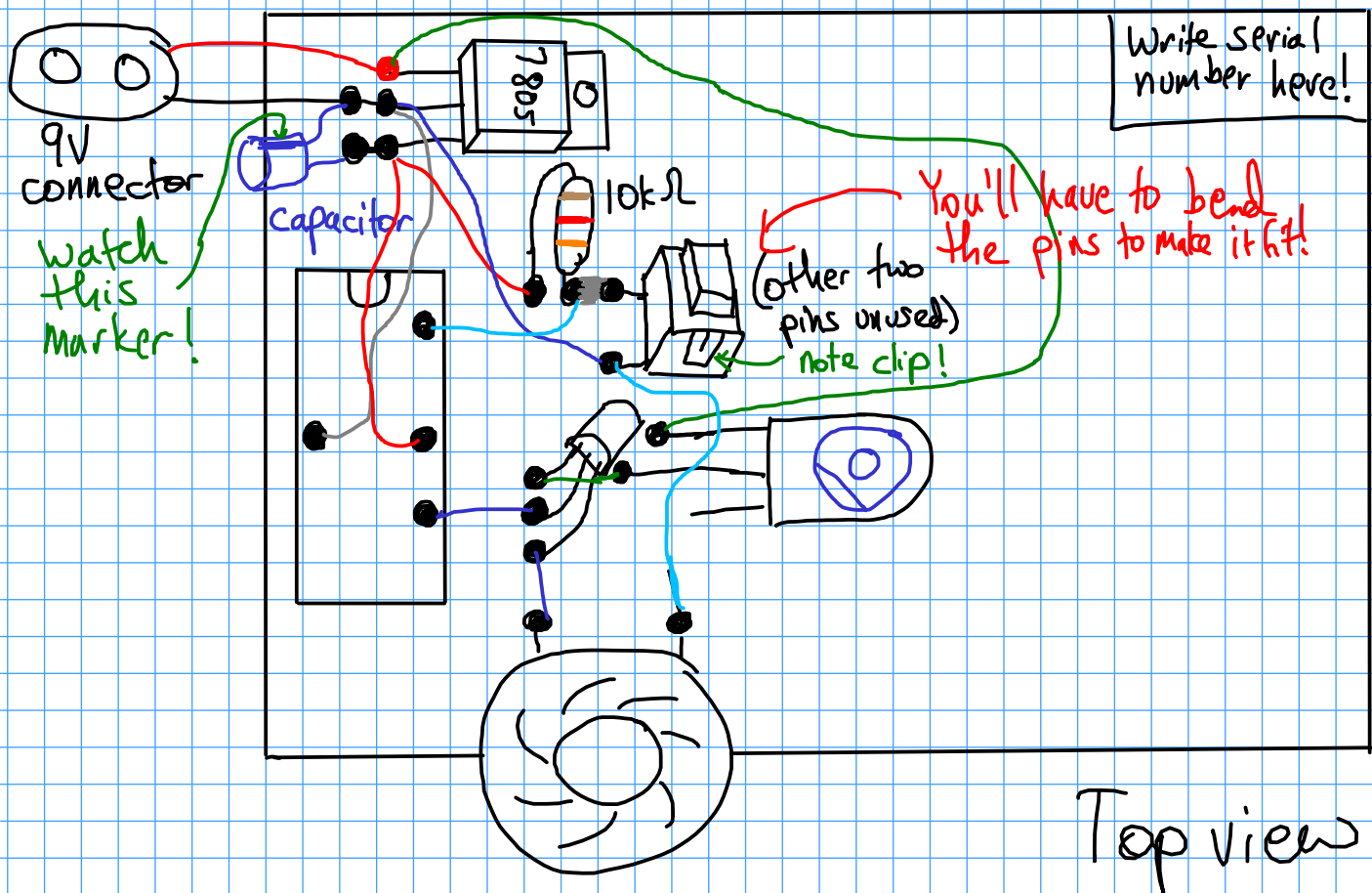


18 October 2010: Audio Reference Transmitter



Suggested work flow:

- ① 7805
- ② Capacitor
- ③ battery connector
- ④ IC socket (hold down with tape, apply solder to 2+ pins to anchor)
- ⑤ Switch
- ⑥ Resistor
- ⑦ Potentiometer
- ⑧ Speaker
- ⑨ Transistor

Either:

Ⓐ Stuff and anchor all parts first, add connections later  
— or —

Ⓑ Add parts and all their connections one at a time

In either case, test connections with an ohmmeter after finishing